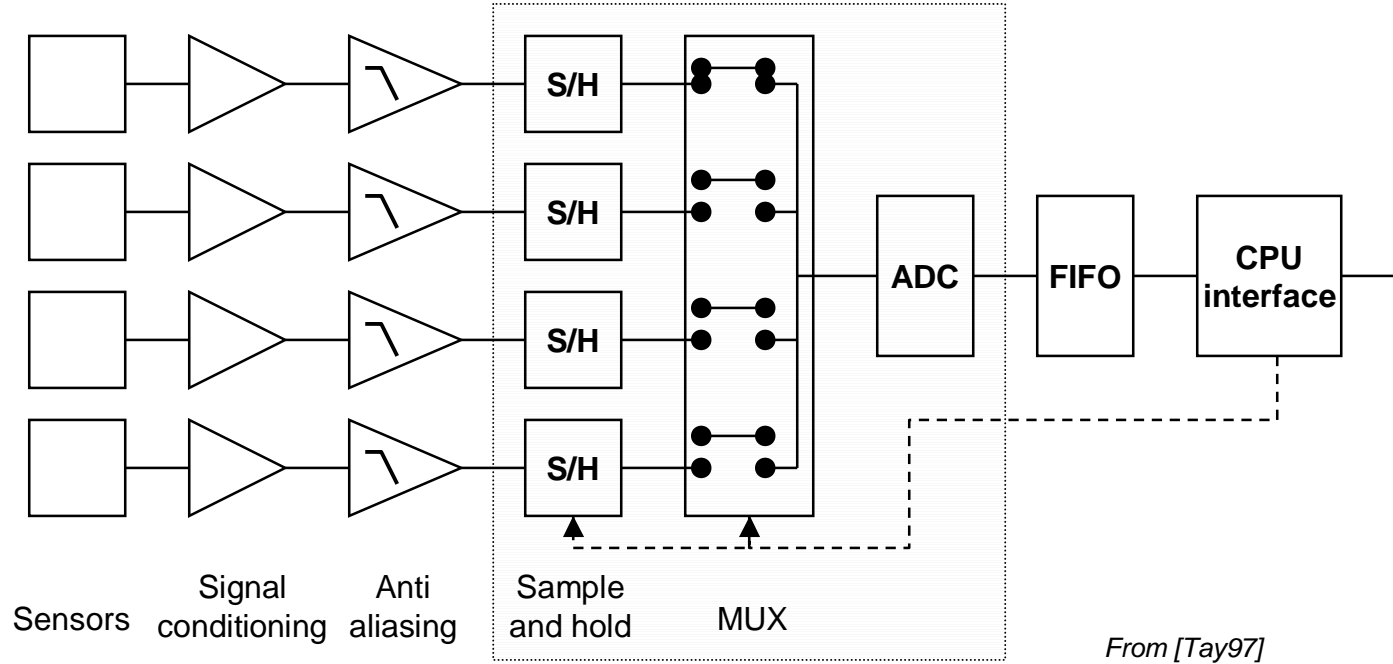


Lecture 8: Data Acquisition II

- **Sample and hold**
- **Multiplexing**
- **Analog to digital conversion**
- **Digital to analog conversion**



Architecture of data acquisition systems




Lecture 8



Sample and hold

- A Sample and hold (S/H) circuit has two basic operating modes
 - **Sample mode:** The output follows the input
 - **Hold mode:** The output is held constant until sample mode is resumed

 - The main application of S/H circuits is to hold the input signal to an ADC constant during conversion
 - Why? Imagine trying to photograph a moving object!




From [FB00]



Basic S/H circuit

■ Basic elements

- Voltage followers
- FET switch

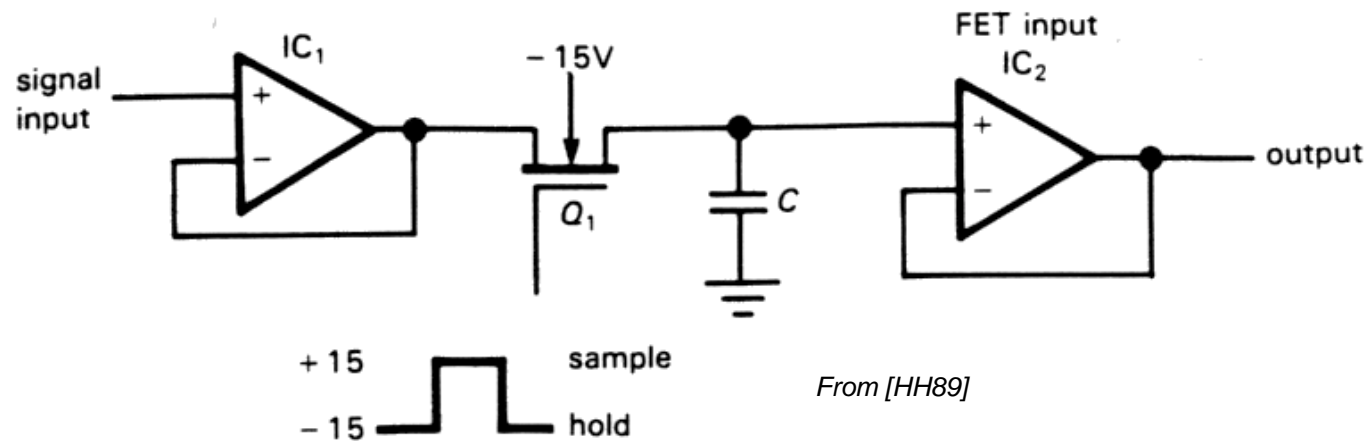

■ Operation


- IC1 provides low Z_{out} version of input signal
- Q1 passes the signal during 'sample' and disconnects during 'hold'
- C preserves the value during 'hold'
- IC2 is a high Z_{in} op-amp to minimize capacitor discharge during 'hold'



S/H response characteristics

■ Response parameters

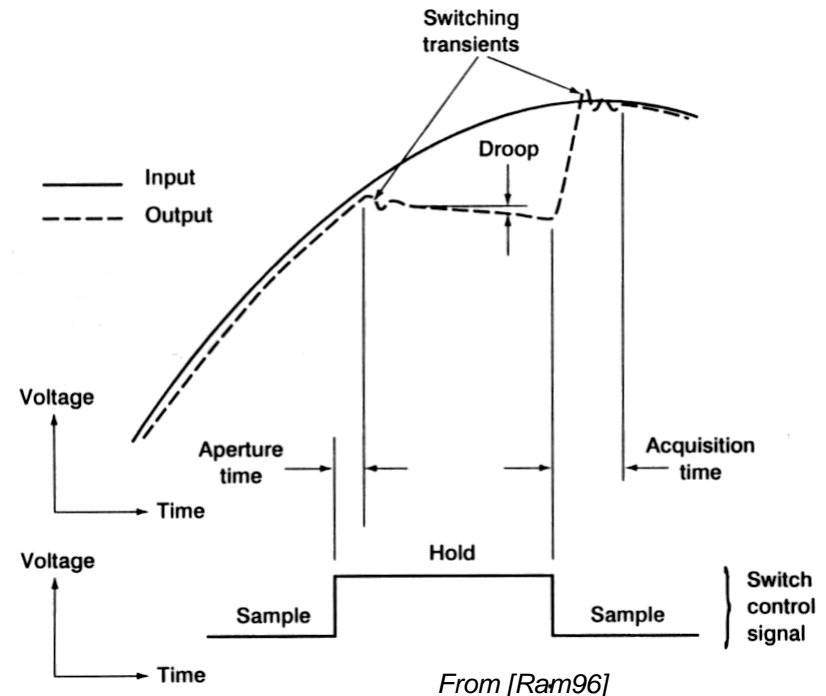- Aperture time: time required for the switch to open (~50ns)
- Droop: capacitor discharge
- (~1mV/ms)
- Acquisition time: switch operation plus capacitor charging time




■ Considerations for choosing C

- C should be large enough to minimize 'droop' caused by leakage currents in Q1 and IC2
- C should be small enough to track fast signals since it forms a low-pass filter with Q1's ON resistance!
 - In practice, the slew rate of the entire circuit is determined by IC1's output current and Q1's ON resistance




Multiplexers

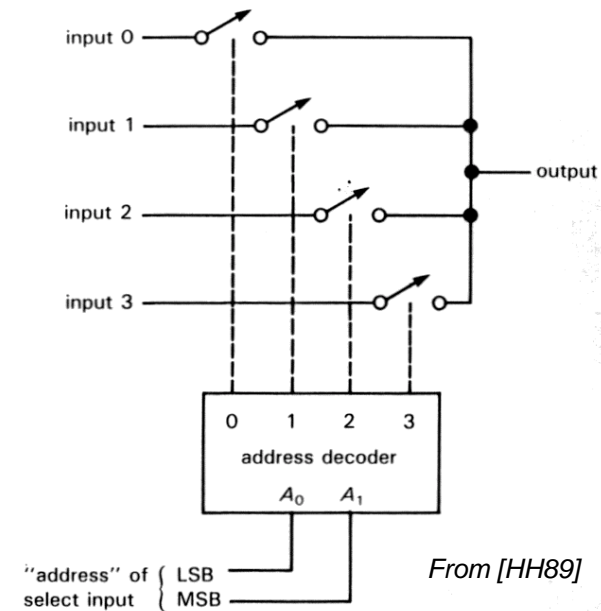- A multiplexer is a circuit that allows you to select any of several inputs, as specified by digital control signals
 - Since analog switches are bi-directional, this circuit could also be used as a de-multiplexer!
 - It could also be used as a digital MUX since logic levels are just voltages



■ FET analog switches

 - N-channel enhancement-mode MOS-FET
 - When Gate is grounded or negative, the FET is non-conducting
 - Drain-source resistance in the order of 10,000M Ω
 - Bringing the Gate to +15V puts the drain-source channel into conduction
 - Drain-source resistance in the order of 100 Ω



Analog-to-digital converters


- **Single slope or ramp**
- **Successive approximation**
- **Dual slope**
- **Parallel or 'flash'**



Single slope or ramp ADC

■ Composed of three basic elements

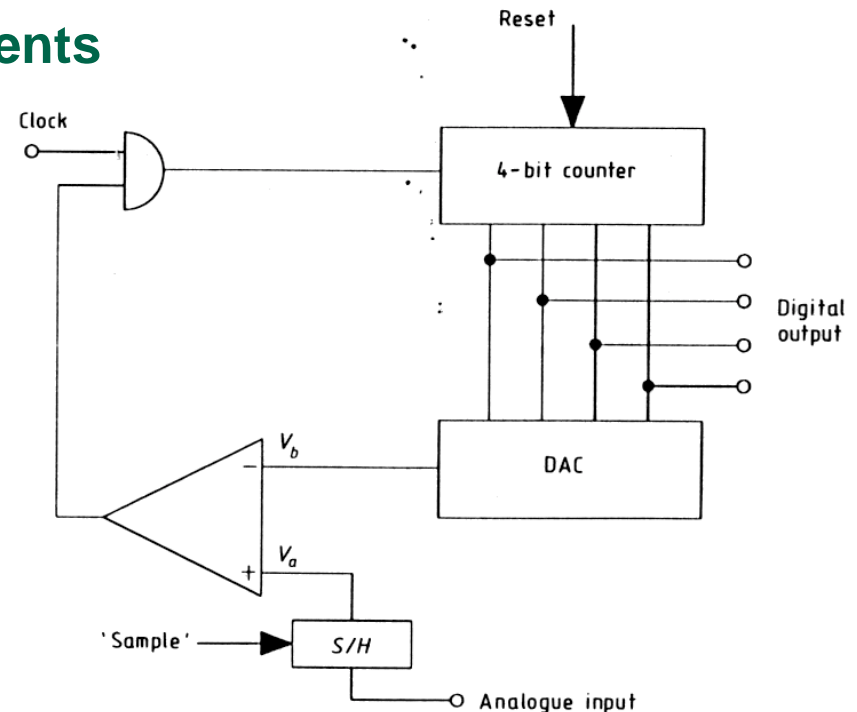- A binary counter
- A digital-to-analog converter
- An analog comparator



From [BW96]

■ Operation

- Counter is reset
- Analog input is sampled
- While $V_A > V_B$ counter increments
- When $V_A = V_B$ counter stops and binary code is available at the output

■ Characteristics


- Relatively slow since conversion time could be up to 2^N , where N is the resolution of the ADC



Successive approximation ADC

■ Basic elements

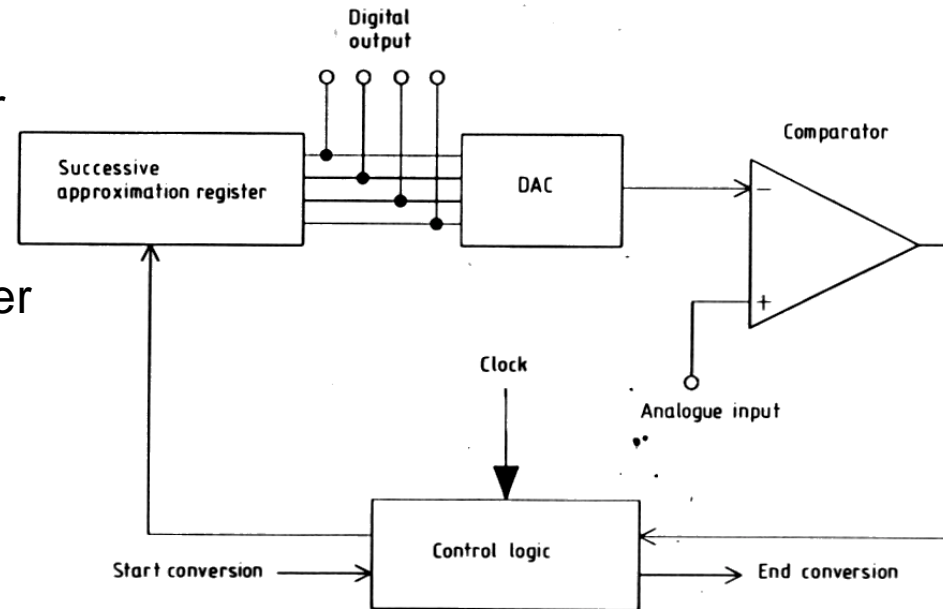- A digital-to-analog converter
- An analog comparator
- A control logic module
- A successive approx. register



From [BW96]

■ Operation is based on a binary search

- Initially, the register provides an output corresponding to half the range (1000...0)
 - If the analog input is greater, then MSB=1, else MSB=0
- The register performs the same operation from MSB to LSB

■ Characteristics

- Conversion requires only N steps, where N is the resolution of the ADC
 - Conversion times of μs are typical



Dual slope ADC

■ Basic elements

- An integrator
- A zero-crossing detector
- A binary counter
- Logic gates and switches

■ Operation



- Counter is reset and switch is connected to the analog input
 - The integrator generates a negative ramp whose slope is proportional to the analog input
 - The comparator goes HIGH, enabling clock pulses into the counter
- When counter overflows, it resets to zero and the control circuit switches the switch to a reference negative voltage
 - This causes the integrator to generate a positive slope ramp
 - When this ramp reaches zero, the comparator goes low and stops the counter, whose value represents the analog input

■ Characteristics

- Very high resolution, but also slower (30 conversions/sec)
 - Widely used in digital multi-meters
- Insensitive to clock drift, RC drifts and high-frequency noise



Dual slope ADC

 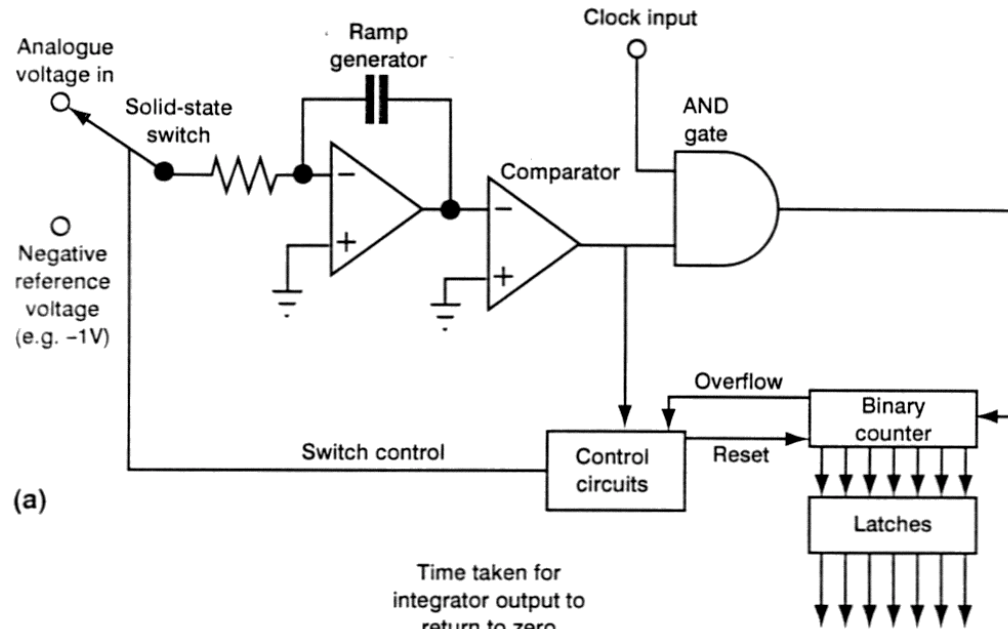

From [Ram96]



Parallel or flash ADC

■ Basic elements

- A multiple voltage divider
- A set of comparators
- A priority encoder

■ Operation


- Analog input applied to all comparators
- Priority encoder converts comparator pattern into binary

■ E.g.: A 3-bit ADC:

- For comparator outputs of 0001111, priority encoder generates 100
- For comparator outputs of 0111111, priority encoder generates 110

■ Characteristics

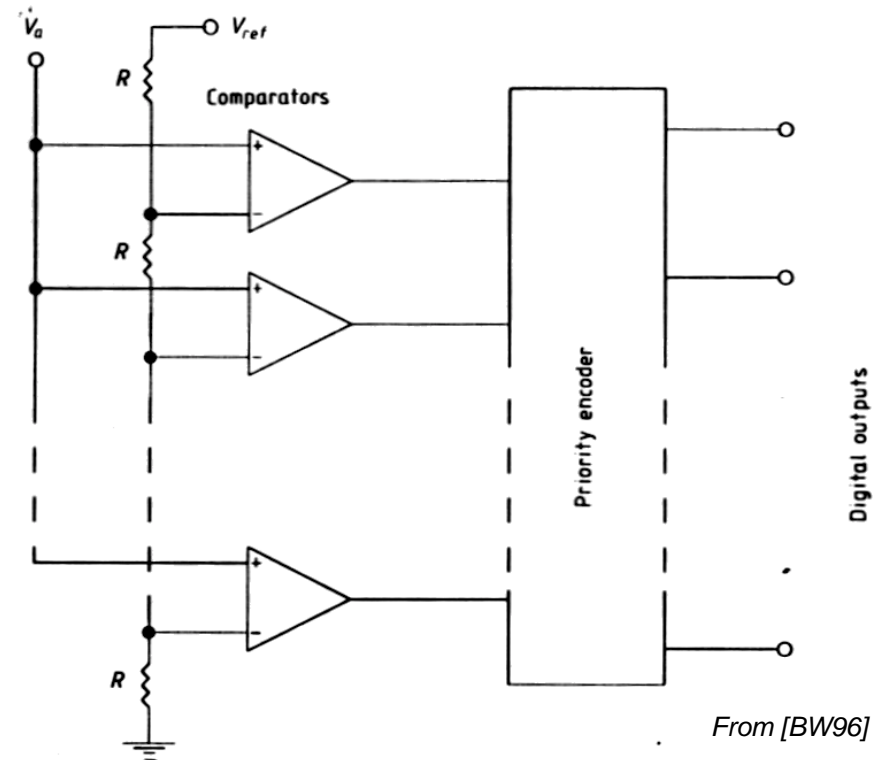- Very fast (e.g., 8-bit ADCs capable of 20 million conversions/sec)
- Very expensive for large N since the number of comparators is $2^N - 1$



Digital-to-analog converters

- Binary weighted ladder
- R-2R ladder
- Pulse width modulation




Binary weighted ladder

■ Based on the summing op-amp circuit from lecture 5

- Each input resistor is twice the value of the previous one
- Inputs are weighted according to their resistors

■ Characteristics

 
- The lowest value resistor R affects the MSB and must have the highest precision
- This circuit is impractical for large N since it would require high precision resistors for a wide range



R-2R ladder

■ Basic elements

- 2N resistors
- An op-amp
- N switches

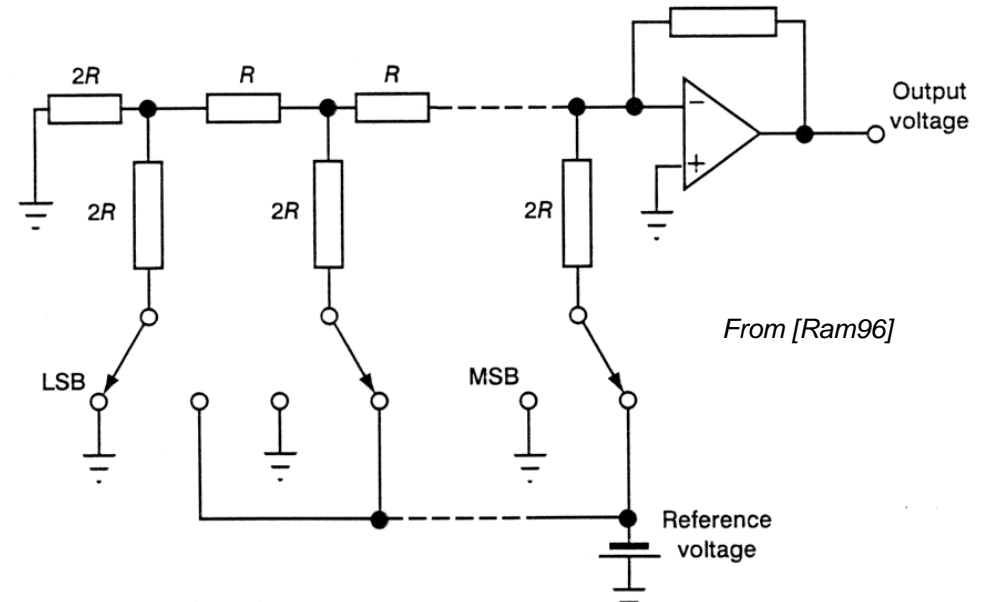

■ Operation


- Switches
 - When bit $I_k=1$, the corresponding switch is connected to V_{REF}
 - When bit $I_k=0$, the corresponding switch is connected to GND
- Assume all the legs but one are grounded
 - The one connected to V_{REF} will generate a current that flows towards the inverting input of the op-amp
 - This current is halved by the resistor network at each node
 - Therefore, the current contribution of each input is weighted by its position in the binary number



R-2R ladder

■ The R-2R operation is better understood by redrawing the resistor network

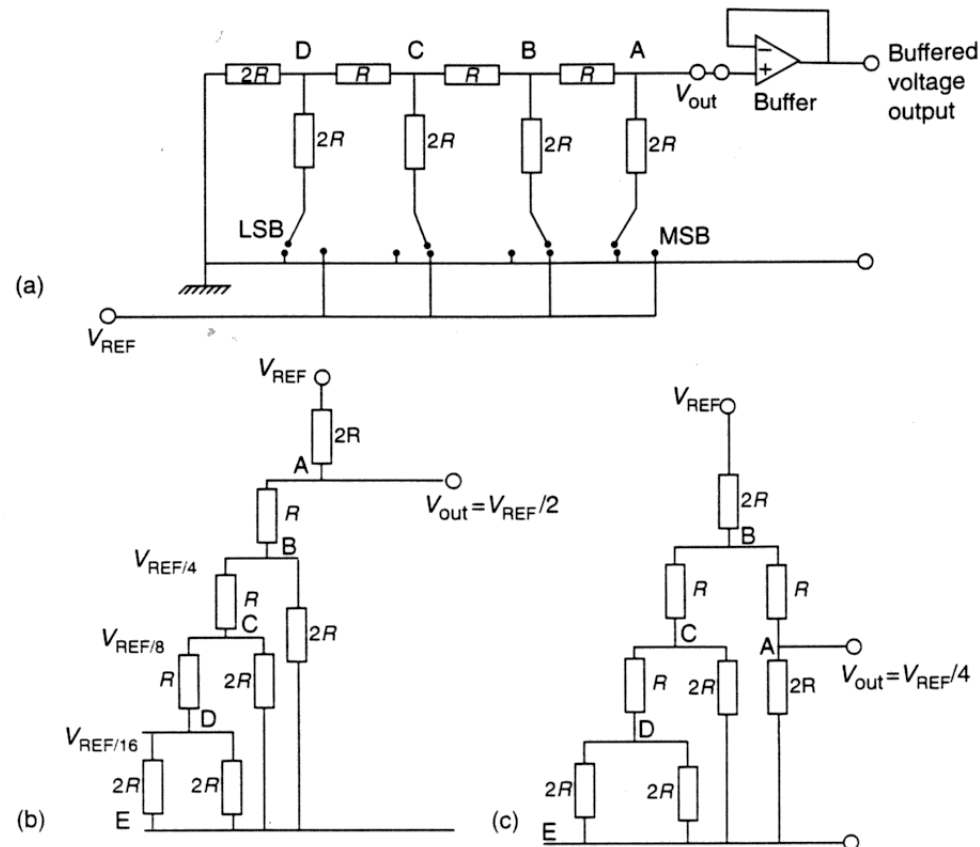- In (b) only the MSB is ON
- In (c) only the next bit to the MSB is ON



From [Tay97]




Pulse Width Modulation

■ Basic components

- A digital line
- An RC low-pass filter

■ Operation

 - The digital line is used to generate a train of pulses of fixed frequency
- The width (duty cycle) of the pulse is made proportional to the desired analog output
- The pulse train is then passed through a low-pass filter, which generates an output voltage proportional to the average time spent in the HIGH state



References

- [Ram96] D. C. Ramsay, 1996, Principles of Engineering Instrumentation, Arnold, London, UK
- [Tay97] H. R. Taylor, 1997, Data Acquisition for Sensor Systems, Chapman and Hall, London, UK.
- [HH89] P. Horowitz and W. Hill, 1989, The Art of Electronics, 2nd Ed., Cambridge University Press, Cambridge, UK
- [BW96] J. Brignell and N. White, 1996, Intelligent Sensor Systems, 2nd Ed., IOP, Bristol, UK.
- [FB00] R. S. Figliola and D.E. Beasley, Theory and design of Mechanical Measurements, 3rd Ed., Wiley, New York.

